

NEC 304

STLD

Lecture 15

Magnitude Comparators and Multiplexers

Rajeev Pandey

Department Of ECE


rajeevvce2007@gmail.com

Overview


- **Discussion of two digital building blocks**
- **Magnitude comparators**
 - Compare two multi-bit binary numbers
 - Create a single bit comparator
 - Use repetitive pattern
- **Multiplexers**
 - Select one out of several bits
 - Some inputs used for selection
 - Also can be used to implement logic

Magnitude Comparator

 - The comparison of two numbers
 - outputs: $A > B$, $A = B$, $A < B$
- Design Approaches
 - the truth table
 - 2^{2n} entries - too cumbersome for large n
 - use inherent regularity of the problem
 - reduce design efforts
 - reduce human errors



Magnitude Comparator

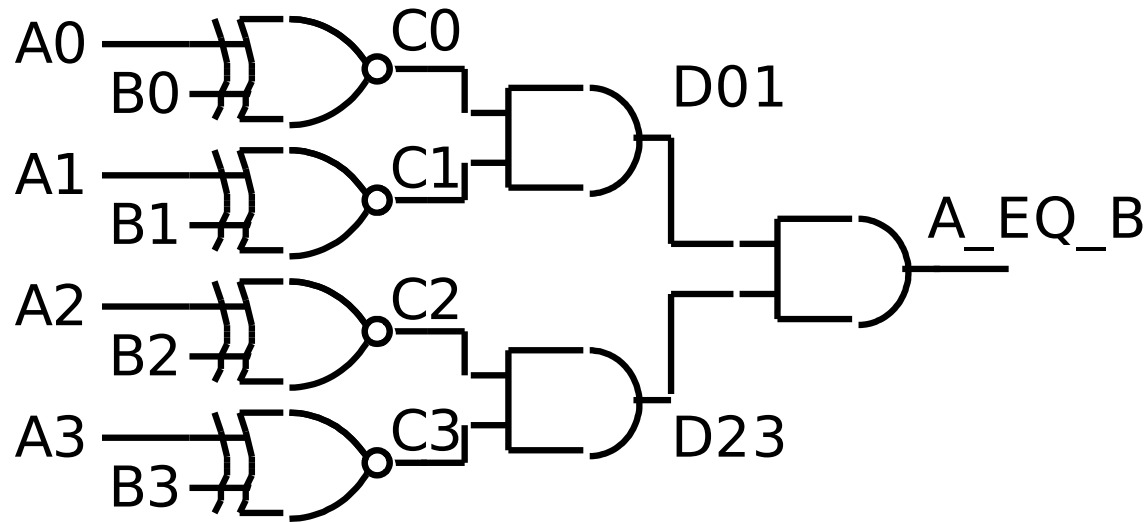


How can we find $A > B$?

How many rows would a truth table have?

$$2^8 = 256$$

Magnitude Comparator

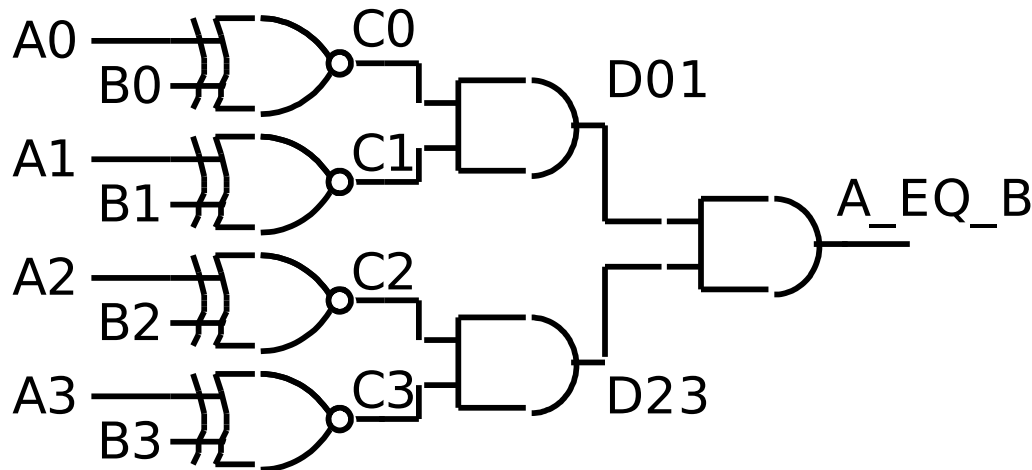

Find $A > B$

If $A = 1001$ and
 $B = 0111$
is $A > B$?

Why?

Because $A3 > B3$
i.e. $A3 \cdot B3' = 1$

Therefore, one term in the
logic equation for $A > B$ is
 $A3 \cdot B3'$

Magnitude Comparator

If $A = 10\textcolor{red}{1}0$ and

$B = 100\textcolor{red}{1}$

is $A > B$?

Why?

$$\begin{aligned} A > B &= A_3 \cdot B_3' \\ &+ C_3 \cdot A_2 \cdot B_2' \\ &+ \dots \end{aligned}$$

Because $A_3 = B_3$ and

$A_2 = B_2$ and

$\textcolor{red}{A_1} > \textcolor{red}{B_1}$

i.e. $C_3 = 1$ and $C_2 = 1$ and

$$A_1 \cdot B_1' = 1$$

Therefore, the next term in the logic equation for $A > B$ is

$$C_3 \cdot C_2 \cdot A_1 \cdot B_1'$$

Magnitude Comparison

- **Algorithm -> logic**

- $A = A_3A_2A_1A_0$; $B = B_3B_2B_1B_0$
- $A=B$ if $A_3=B_3$, $A_2=B_2$, $A_1=B_1$ and $A_0=B_0$

- **Test each bit:**


- equality: $x_i = A_iB_i + A_i'B_i'$
- $(A=B) = x_3x_2x_1x_0$

- **More difficult to test less than/greater than**

- $(A>B) = A_3B_3' + x_3A_2B_2' + x_3x_2A_1B_1' + x_3x_2x_1A_0B_0'$
- $(A<B) = A_3'B_3 + x_3A_2'B_2 + x_3x_2A_1'B_1 + x_3x_2x_1A_0'B_0$
- Start comparisons from **high-order** bits

- **Implementation**

- $x_i = (A_iB_i' + A_i'B_i)'$

 

TRUTH TABLE

| COMPARING INPUTS | | | | CASCADING INPUTS | | | OUTPUTS | | |
|---------------------------------|---------------------------------|---------------------------------|---------------------------------|---------------------|---------------------|------------------|---------------------|---------------------|------------------|
| A ₃ , B ₃ | A ₂ , B ₂ | A ₁ , B ₁ | A ₀ , B ₀ | I _{A>B} | I _{A<B} | I _{A=B} | O _{A>B} | O _{A<B} | O _{A=B} |
| A ₃ > B ₃ | X | X | X | X | X | X | H | L | L |
| A ₃ < B ₃ | X | X | X | X | X | X | L | H | L |
| A ₃ = B ₃ | A ₂ > B ₂ | X | X | X | X | X | H | L | L |
| A ₃ = B ₃ | A ₂ < B ₂ | X | X | X | X | X | L | H | L |
| A ₃ = B ₃ | A ₂ = B ₂ | A ₁ > B ₁ | X | X | X | X | H | L | L |
| A ₃ = B ₃ | A ₂ = B ₂ | A ₁ < B ₁ | X | X | X | X | L | H | L |
| A ₃ = B ₃ | A ₂ = B ₂ | A ₁ = B ₁ | A ₀ > B ₀ | X | X | X | H | L | L |
| A ₃ = B ₃ | A ₂ = B ₂ | A ₁ = B ₁ | A ₀ < B ₀ | X | X | X | L | H | L |
| A ₃ = B ₃ | A ₂ = B ₂ | A ₁ = B ₁ | A ₀ = B ₀ | H | L | L | H | L | L |
| A ₃ = B ₃ | A ₂ = B ₂ | A ₁ = B ₁ | A ₀ = B ₀ | L | H | L | L | H | L |
| A ₃ = B ₃ | A ₂ = B ₂ | A ₁ = B ₁ | A ₀ = B ₀ | X | X | H | L | L | H |
| A ₃ = B ₃ | A ₂ = B ₂ | A ₁ = B ₁ | A ₀ = B ₀ | L | L | L | H | H | L |
| A ₃ = B ₃ | A ₂ = B ₂ | A ₁ = B ₁ | A ₀ = B ₀ | H | H | L | L | L | L |


H = HIGH Voltage Level

L = LOW Voltage Level

X = Immaterial


Magnitude Comparator

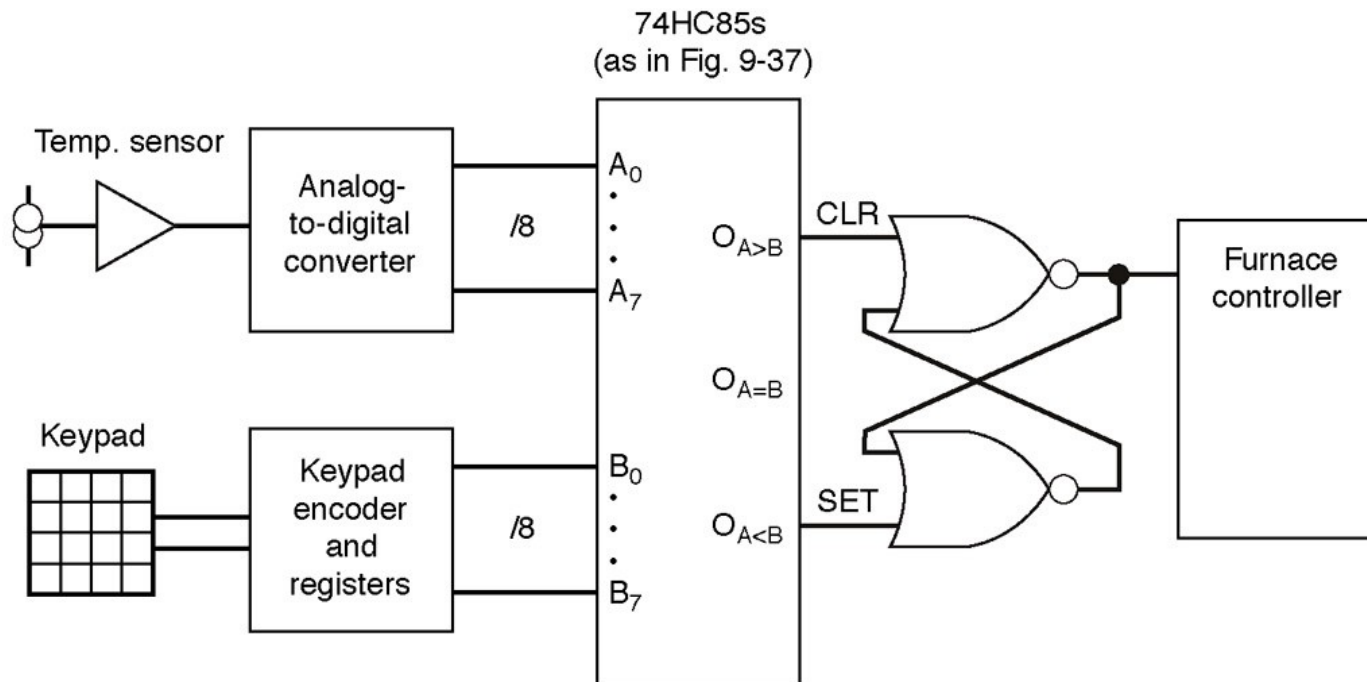- Real-world application
 - Thermostat controller




Multiplexers

 - Select an input value with one or more select bits
- Use for transmitting data
- Allows for **conditional** transfer of data
- Sometimes called a **mux**




(a) Logic diagram

 


(b) Block diagram

Fig. 4-24 2-to-1-Line Multiplexer

4- to- 1- Line Multiplexer

 

Quadruple 2-to-1-Line Multiplexer

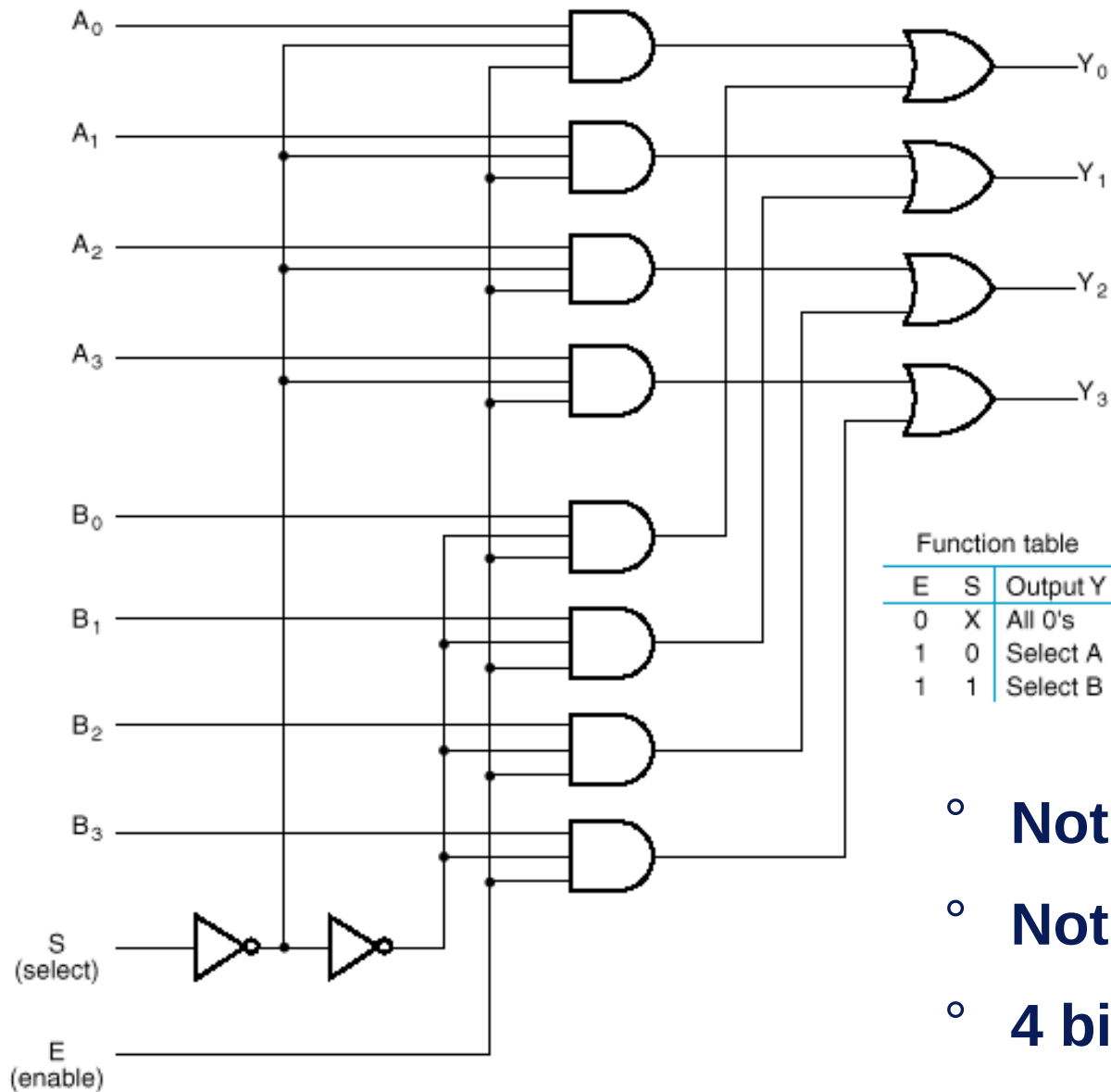


Multiplexer as combinational modules

- Connect input variables to select inputs of multiplexer ($n-1$ for n variables)
- Set data inputs to multiplexer equal to values of function for corresponding assignment of select variables
- Using a variable at data inputs reduces size of the multiplexer

| x | y | z | F |
|-----|-----|-----|-----|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 |

(a) Truth table

 


(b) Multiplexer implementation

Fig. 4-27 Implementing a Boolean Function with a Multiplexer

Implementing a Four- Input Function with a Multiplexer

| A | B | C | D | F | |
|---|---|---|---|---|---------------|
| 0 | 0 | 0 | 0 | 0 | $F = D$ |
| 0 | 0 | 0 | 1 | 1 | |
| 0 | 0 | 1 | 0 | 0 | $F = D$ |
| 0 | 0 | 1 | 1 | 1 | |
| 0 | 1 | 0 | 0 | 1 | $F = \bar{D}$ |
| 0 | 1 | 0 | 1 | 0 | |
| 0 | 1 | 1 | 0 | 0 | $F = 0$ |
| 0 | 1 | 1 | 1 | 0 | |
| 1 | 0 | 0 | 0 | 0 | $F = 0$ |
| 1 | 0 | 0 | 1 | 0 | |
| 1 | 0 | 1 | 0 | 0 | $F = D$ |
| 1 | 0 | 1 | 1 | 1 | |
| 1 | 1 | 0 | 0 | 1 | $F = 1$ |
| 1 | 1 | 0 | 1 | 1 | |
| 1 | 1 | 1 | 0 | 1 | $F = 1$ |
| 1 | 1 | 1 | 1 | 1 | |

 

Typical multiplexer uses


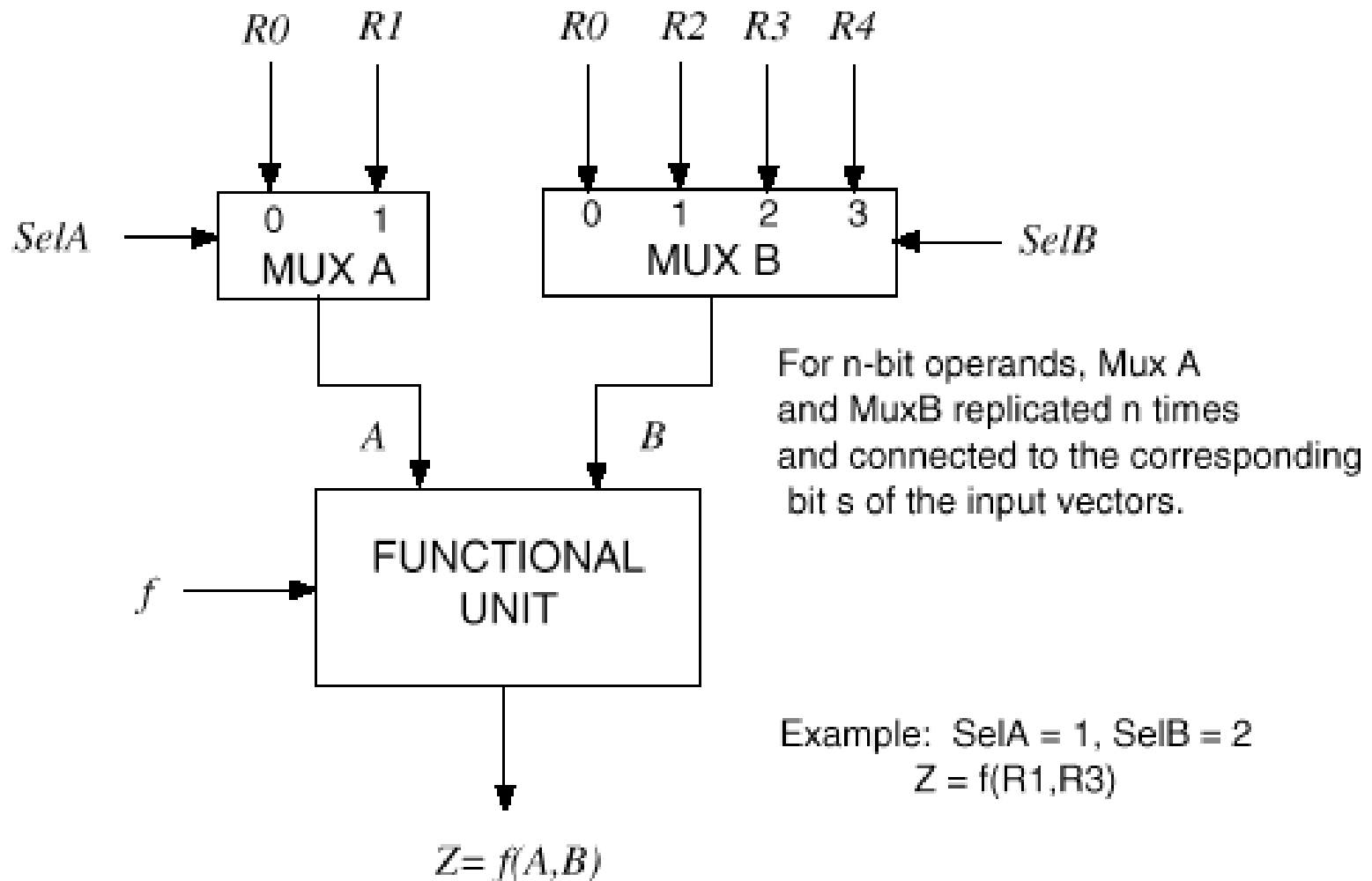


Figure 9.21: Multiplexer example of use.

Three-state gates

 
- A multiplexer can be constructed with three-state gates
- Output state: 0, 1, and high-impedance (open ckts)
- If the select input (E) is 0, the three-state gate has **no output**



Opposite true here,
No output if \bar{E} is 1

| \bar{E} | x |
|-----------|------|
| 0 | A |
| 1 | Hi-Z |

(a)

 


| E | x |
|---|------|
| 0 | Hi-Z |
| 1 | A |


(b)

Three-state gates

 - A multiplexer can be constructed with three-state gates
- Output state: 0, 1, and high-impedance (open cks)
- If the select input is low, the three-state gate has **no output**



(a) 2-to-1- line mux

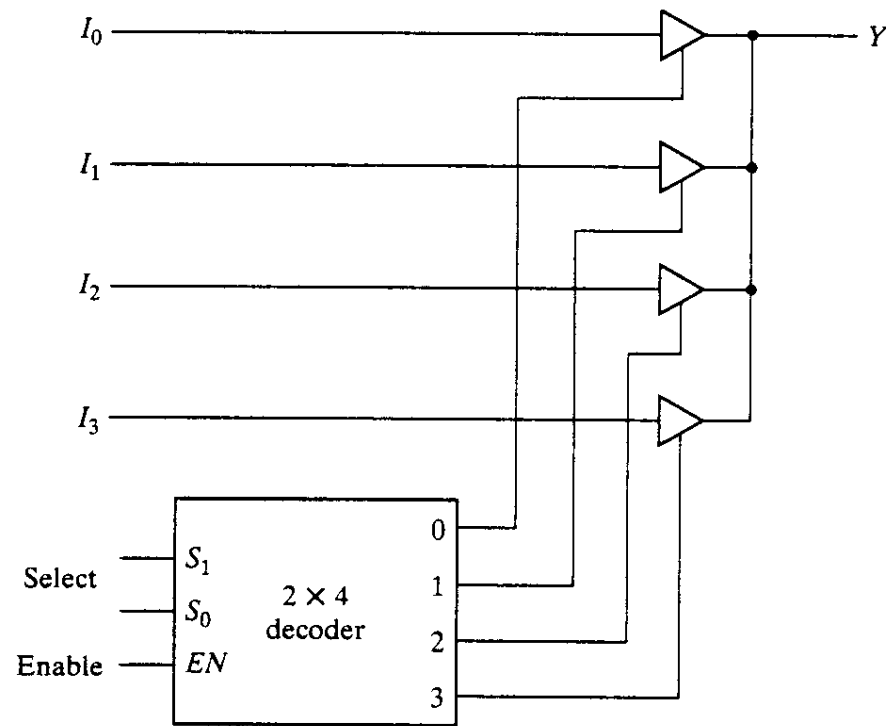

(b) 4 - to - 1 line mux

Summary

- **Magnitude comparators allow for data comparison**
 - Can be built using and-or gates
- **Greater/less than requires more hardware than equality**
- **Multiplexers are fundamental digital components**
 - Can be used for logic
 - Useful for **datapaths**
 - Scalable
- **Tristate buffers have three types of outputs**
 - 0, 1, high-impedence (Z)
 - Useful for datapaths